

DAY 5

FULL ADDER


The full-adder accepts two input bits and an input carry and generates a sum output and an output carry.

The basic difference between a full-adder and a half-adder is that the full-adder accepts an input carry.

Truth Table


A	B	Cin	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Diagram

 

Gate level
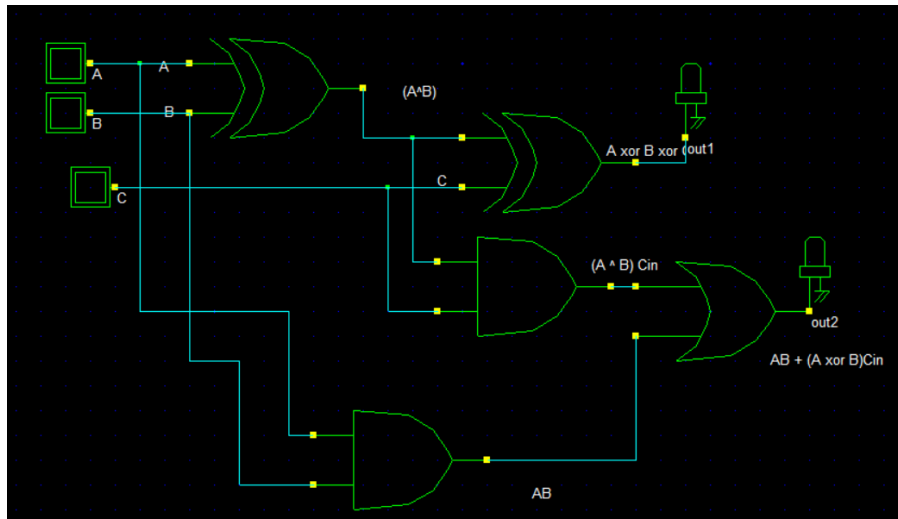
```
module Full_Addder( A,B,Cin,Sum,Carry);  
  input A,B,Cin;  
  output Sum,Carry;  
  wire w1,w2,w3,w4,w5;  
  xor G1(w1,A,B);  
  xor G2(w2,w1,Cin);  
  and G3(w3,w1,Cin);  
  and G4(w4,A,B);  
  or G5(w5,w4,w3);  
endmodule
```



Dataflow

```
module Adder(A,B,Sum,Carry,Cin);  
    input A,B,Cin;  
    output Sum,Carry;  
    assign Sum = (A^B^Cin);  
    assign Carry = ((A&B)|(A^B)&Cin);  
endmodule
```

Behavioral

```
module Adder(A,B,Cin,Sum,Cout);  
    input A,B,Cin;  
    output Sum,Cout;  
    reg Sum,Cout;  
    always @(A,B,Cin)  
    begin  
        Sum = (A^B^Cin);  
        Carry = ((A&B)|(A^B)&Cin);  
    end  
endmodule
```

Simulation Waveform

