

DAY – 4

HALF ADDER

Theory : -

A half adder is a fundamental digital circuit used in computer hardware and digital electronics to perform basic binary addition. It adds two single-digit binary numbers and produces two outputs: the sum (S) and the carry (C). Half adders are essential building blocks for more complex arithmetic circuits like full adders, which can add multiple bits.

Here's some information about a half adder:

Inputs:

A: The first binary input digit (0 or 1).

B: The second binary input digit (0 or 1).

Outputs:

1. **Sum (S):** This output represents the least significant bit of the addition result. The sum is obtained by taking the XOR (exclusive OR) of A and B. $S = A \text{ XOR } B$
2. **Carry (C):** This output represents the carry-out of the addition operation. The carry is obtained by taking the AND operation of A and B. $C = A \text{ AND } B$


Truth Table: The following truth table summarizes the behavior of a half adder

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	1	1

Logical Equations: The logical equations for the sum (S) and carry (C) can be expressed as follows:

1. Sum (S) = $A \text{ XOR } B$
2. Carry (C) = $A \text{ AND } B$

Circuit Diagram

 

Gate Modelling

```
module HalfAdder(A,B,Sum,Carry);  
  input A,B;  
  output Sum,Cary;  
  xor G1(Sum,A,B);  
  and G2 (Carry,A,B);  
endmodule
```

DataFlow Modelling

```
module HalfAdder(A,B,Sum,Carry);  
  input A,B;  
  output Sum,Carry;  
  assign Sum = (A ^ B);  
  assign Carry = (A && B);  
endmodule
```

Behavioral Modelling

```
module HalfAdder(A,B,Sum,Carry);
```

```
input A,B;
```

```
output Sum,Carry;
```

```
always @(A,B)
```

```
begin
```

```
case ({A,B})
```

```
3'b00: sum = 0;
```

```
3'b01: sum = 1;
```

```
3'b10: sum = 1;
```

```
3'b11: sum = 0;
```

```
default : sum = 0;
```

```
endcase
```

```
case ({A,B})
```

```
3'b00: cout = 0;
```

```
3'b01: cout = 0;
```

```
3'b10: cout = 0;
```

```
3'b11: cout = 1;
```





```
default : cout = 0;
```

```
endcase
```

```
end
```

```
endmodule
```

Dsch – Using Xor and AND

    

Simulation waveform:

