

DAY – 6

HALF SUBTRACTOR

Theory :-


The half subtractor is a building block for subtracting two binary numbers. It has the following characteristics:

Two inputs, A and B

Two outputs, Difference and Borrow

The Difference output is the resultant of the Exclusive-OR gate

Circuit Diagram

 

Expression

$$D = A \oplus B$$


$$\text{Bout} = A' B;$$

Truth Table

A	B	Dout	Bout
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0


Verilog Code using Gate Level:
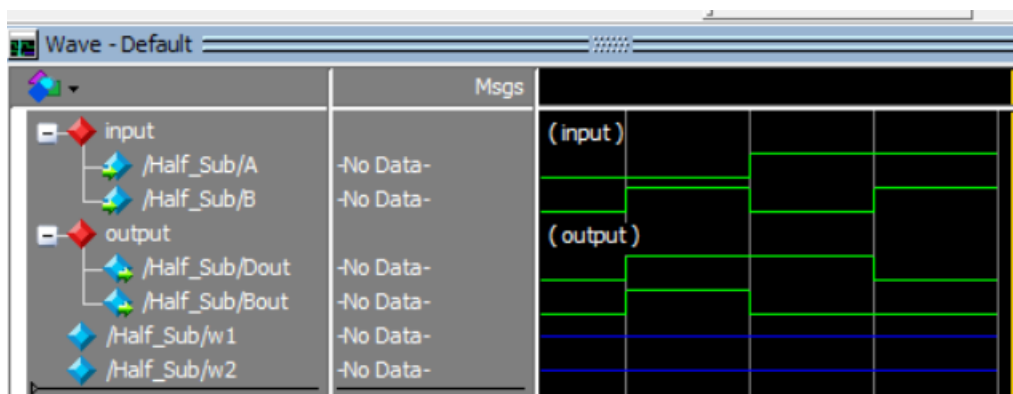
```
module Half_Sub(A,B,Dout,Bout);  
  input A,B;  
  output Dout,Bout;  
  wire w1,w2;  
  xor g1(Dout,A,B);  
  and g2(Bout, ~A, B);  
endmodule
```



Data Flow
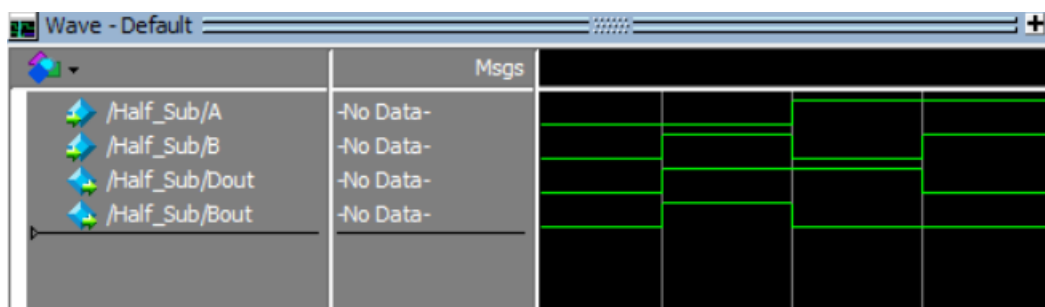
```
module Half_Sub(A,B Dout,Bout);  
  input A,B;  
  output Dout,Bout;  
  assign Dout = (A^B);  
  assign Bout = (~A & B);  
endmodule
```



Behavioral

```
module half_subtractor( A,B,Dout,Bout);
```

```
input A,B;
```

```
output reg Dout,Bout;
```

```
always @(*)
```

```
begin
```

```
    Dout = A^B;
```

```
    Bout = (~A) & B ;
```

```
end
```

```
endmodule
```

